

Course „Control Systems 2“

Exercise Sheet 1

Task 1:

An RLC network is shown in the figure below. Define the state variables as $x_1 = i_L$ and $x_2 = u_C$. Moreover, assume that the inputs are the source voltages and that the output is the current through the resistor. Determine the state equations.

