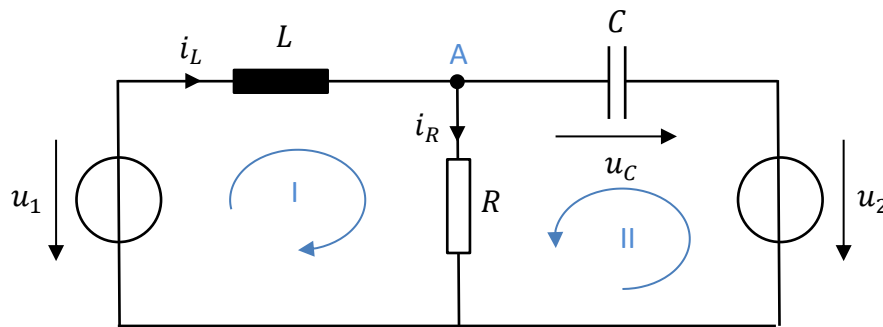


Course „Control Systems 2“

Solution to Exercise Sheet 1

Task 1: Solution

- Physical modelling:



- mesh rules:

$$(I) \quad u_1 = L \frac{di_L}{dt} + Ri_R \quad (1)$$

$$(II) \quad u_2 = -u_C + Ri_R \quad (2)$$

- junction rule at point A:

$$i_L - i_R - C \frac{du_C}{dt} = 0 \quad (3)$$

- using (3) we can eliminate i_R (note that i_R must not be present on the right-hand side of the state equations, since it is neither state nor input):

$$(3) \rightarrow i_R = i_L - C \frac{du_C}{dt}$$

- substitute this expression in (1) and (2):

$$(1) \rightarrow u_1 = L \frac{di_L}{dt} + Ri_L - RC \frac{du_C}{dt} \quad (4)$$

$$(2) \rightarrow u_2 = -u_C + Ri_L - RC \frac{du_C}{dt} \quad (5)$$

- Introduce state variables and solve for time-derivatives of the states:

- substitute $i_L = x_1$ and $u_C = x_2$ in (4) and (5):

$$(4) \rightarrow u_1 = L\dot{x}_1 + Rx_1 - RC\dot{x}_2 \quad (6)$$

$$(5) \rightarrow u_2 = -x_2 + Rx_1 - RC\dot{x}_2 \quad (7)$$

- solve for time derivatives \dot{x}_1 and \dot{x}_2 :

$$(7) \rightarrow \dot{x}_2 = \frac{1}{C}x_1 - \frac{1}{RC}x_2 - \frac{1}{RC}u_2 \quad (8)$$

$$(8) \text{ in } (6) \rightarrow \dot{x}_1 = -\frac{1}{L}x_2 + \frac{1}{L}u_1 - \frac{1}{L}u_2 \quad (9)$$

- **Express output in terms of states (x_1 & x_2) and inputs (u_1 & u_2):**

$$(2) \rightarrow i_R = \frac{1}{R}u_C + \frac{1}{R}u_2$$

- using $i_R = y$ and $u_C = x_2$:

$$\rightarrow y = \frac{1}{R}x_2 + \frac{1}{R}u_2 \quad (10)$$

- **Sort equations and summarize:**

- eqs. (9), (8) and (10) are the required state space description of the system:

$$\begin{aligned}\dot{x}_1 &= -\frac{1}{L}x_2 + \frac{1}{L}u_1 - \frac{1}{L}u_2 \\ \dot{x}_2 &= \frac{1}{C}x_1 - \frac{1}{RC}x_2 - \frac{1}{RC}u_2 \\ y &= \frac{1}{R}x_2 + \frac{1}{R}u_2\end{aligned}$$