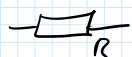


Bilinear Transform and Frequency Warping

(Z-Transform)


Laplace-Transform



$$U(s) = R \cdot I(s)$$



$$U(s) = s \cdot L \cdot I(s)$$

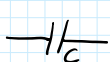

$$U(s) = \frac{1}{sC} \cdot I(s)$$

Steps of the Bilinear Transform:

- 1) Description of the circuit via Laplace-Transform
- 2) Substitute $s \approx G \frac{z-1}{z+1}$ with $G = \frac{2\pi f_0}{\tan(\pi f_0 T)}$

Frequency Warping


T : sampling time

f_0 : frequency at which the approximation is precise:


low-/high-pass filter: cut-off frequency

band pass: center frequency

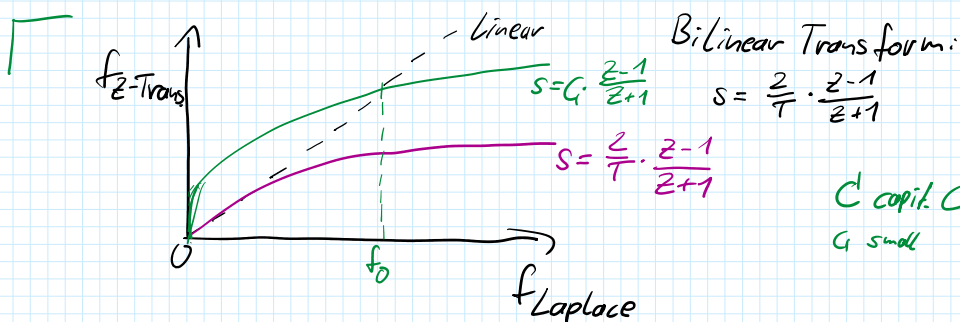\Rightarrow allows a time-discrete realisation of a system.



Example: Series resonant circuit

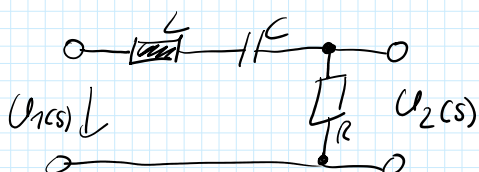

Transfer-Function:

Transfer - Function:

$$H(s) = \frac{U_2(s)}{U_1(s)} = \frac{R}{R + sL + \frac{1}{sC}}$$

resonance frequency $f_0 = ?$

Definition of f_0 : $H(s)$ is completely real valued

$$sL + \frac{1}{sC} = 0 \Rightarrow sL = -\frac{1}{sC} \Rightarrow s^2 LC = -1$$

$$\Rightarrow s^2 = -\frac{1}{LC}$$

$$s = \sigma + j\omega = \sigma + j2\pi f_0$$
$$\sigma = 0$$

$$\Rightarrow (j2\pi f_0)^2 = -\frac{1}{LC}$$

$$(2\pi f_0)^2 = \frac{1}{LC} \Rightarrow f_0 = \frac{1}{2\pi\sqrt{LC}}$$

Determine a time-discrete realisation of the filter by using the bilinear transform.

$$T = \frac{1}{1000} \text{ s} \quad R = 100 \Omega \quad L = 100 \text{ mH} \quad C = 100 \mu\text{F}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = 50,3 \text{ Hz}$$

$$G = \frac{2\pi f_0}{\tan(\pi f_0 T)} = 1983 \text{ Hz}$$

$$H(s) = \frac{R}{R + sL + \frac{1}{sC}} \cdot \frac{sC}{sC} = \frac{sRC}{sRC + s^2LC + 1}$$

Bilinear Transform: $s \approx G \cdot \frac{z-1}{z+1}$

$$H(z) = \frac{G \cdot \frac{z-1}{z+1} \cdot RC}{G \cdot \frac{z-1}{z+1} \cdot RC + G^2 \frac{(z-1)^2}{(z+1)^2} \cdot LC + 1} \cdot \frac{(z+1)^2}{(z+1)^2}$$

$$= \frac{G(z-1)(z+1)RC}{G(z-1)(z+1)RC + G^2(z-1)^2 \cdot LC + (z+1)^2}$$

$$= \frac{GRC(z^2-1)}{GRC(z^2-1) + G^2LC(z^2-2z+1) + (z^2+2z+1)}$$

$$= \frac{GRC'(z^2-1) + G^2LC'(z^2-2z+1) + (z^2+2z+1)}{a_1z^2 + a_2z + a_3}$$

$$b_1 = GRC' = 1983 \text{ Hz} \cdot 100 \Omega \cdot 100 \mu\text{F} = 19,83$$

$$\text{Unit-check: } \frac{1}{s} \cdot \frac{V}{A} \cdot \frac{As}{V} = 1$$

$$b_2 = 0$$

$$b_3 = -GRC' = -19,83$$

$$a_1 = GRC' + G^2LC' + 1 = 60,15$$

$$a_2 = -2G^2LC' + 2 = -76,65$$

$$a_3 = -GRC' + G^2LC' + 1 = 20,49$$

$$\Rightarrow H(z) = \frac{19,83 \cdot z^2 + 0 \cdot z - 19,83}{60,15 \cdot z^2 - 76,65z + 20,49}$$

e.g. look at
Pole-Null-Diagramm

Difference Equation and Block Diagram?


$$H(z) = \frac{Y(z)}{X(z)} = \frac{b_1z^2 + b_2z + b_3}{a_1z^2 + a_2z + a_3} \cdot \frac{z^{-2}}{z^{-2}} = \frac{b_1 + b_2z^{-1} + b_3z^{-2}}{a_1 + a_2z^{-1} + a_3z^{-2}}$$


$$Y(z) \cdot (a_1 + a_2z^{-1} + a_3z^{-2}) = X(z) (b_1 + b_2z^{-1} + b_3z^{-2})$$

Time discrete form


$$a_1 \cdot y(n) + a_2 \cdot y(n-1) + a_3 \cdot y(n-2) = b_1 \cdot x(n) + b_2 \cdot x(n-1) + b_3 \cdot x(n-2)$$
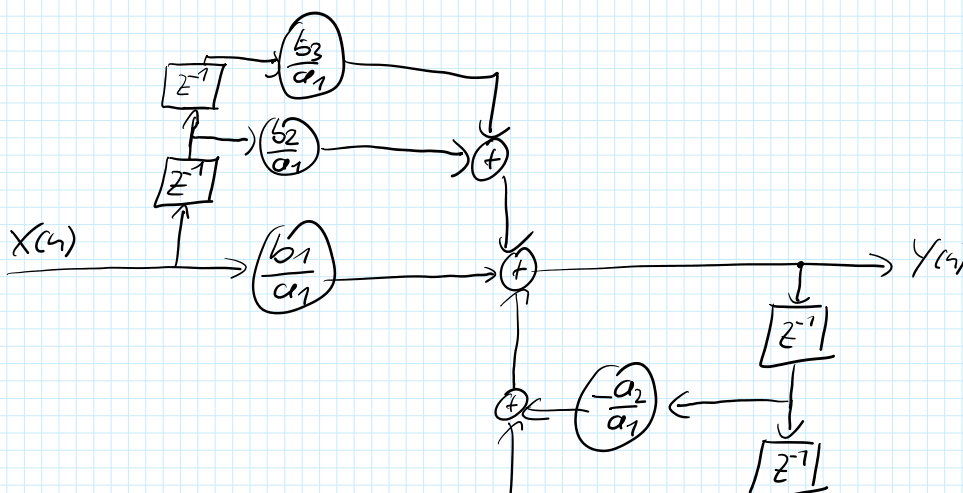
$$y(n) = \frac{b_1}{a_1} x(n) + \frac{b_2}{a_1} x(n-1) + \frac{b_3}{a_1} x(n-2) - \frac{a_2}{a_1} y(n-1) - \frac{a_3}{a_1} y(n-2)$$



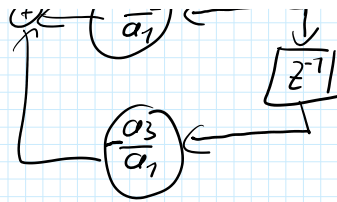

Example: discharge process

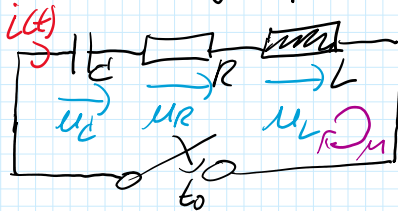

$$u_C(t=0) = 12V$$

$$u_C(t) = \frac{1}{C} \cdot Q(t)$$

$$\begin{aligned} u_R(t) &= R \cdot i(t) \\ &= R \cdot \frac{dQ(t)}{dt} \\ &= R \cdot C \frac{du_C(t)}{dt} \end{aligned}$$

$$u_L(t) = L \cdot \frac{di(t)}{dt} = LC \frac{d^2 u_C(t)}{dt^2}$$

$\mathcal{M}: u_C(t) + u_R(t) + u_L(t) = 0$

$$u_C(t) + RC \frac{du_C(t)}{dt} + LC \frac{d^2 u_C(t)}{dt^2} = 0$$



$$U(s) + RC \cdot s \cdot U(s) + LC \cdot s^2 \cdot U(s) = 0$$

Apply Bilinear Transform: $s \approx G \frac{z-1}{z+1}$

$$U(z) + RC G \frac{z-1}{z+1} U(z) + LC G^2 \frac{(z-1)^2}{(z+1)^2} U(z) = 0 \quad | \cdot (z+1)^2$$

\vdots

$$U(z) [(1 + GRC + G^2 LC) + z^{-1}(2 - 2G^2 LC) + z^{-2}(1 - GRC + G^2 LC)] = 0$$

discrete form

$$u(n) = \frac{-1}{1 + GRC + G^2 LC} [(2 - 2G^2 LC) \cdot u(n-1) + (1 - GRC + G^2 LC) \cdot u(n-2)]$$

$$\Rightarrow \text{Python / Matlab ...} \quad u(0) = 12V$$

$$u(1) = 12V$$